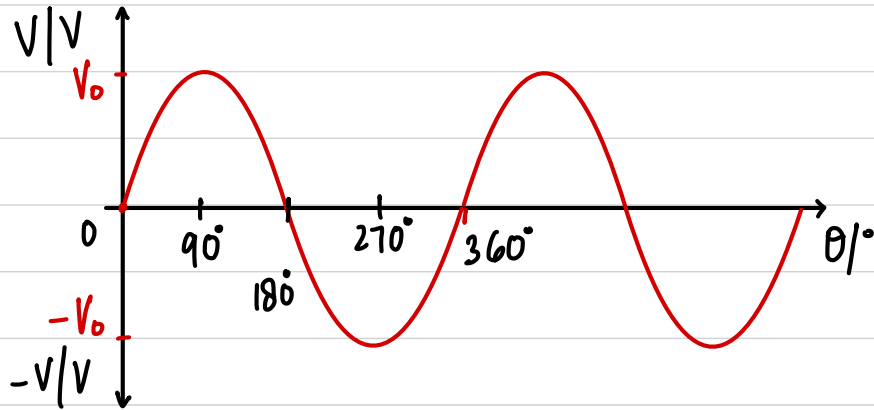


General Equation of Alternating Voltage and Current



$$Y = A \sin BX + C$$

A: Amplitude

B: No. of cycles in 360°

C: y-intercept (mean value)

$$Y: V \quad A: V_0$$

$$X: \theta \quad B: 1$$

$$C: 0$$

$$V = V_0 \sin(1) \theta + 0 \rightarrow V = V_0 \sin \theta$$

$$\omega = \frac{\Delta \theta}{\Delta t}$$

$$\theta_i = 0^\circ$$

$$t_i = 0s$$


$$\omega = \frac{\theta - 0}{t - 0}$$

$$\theta_f = \theta$$

$$t_f = t$$


- ☑ Max Voltage : Coil crosses horizontal
- ☑ Min Voltage : Coil crosses vertical
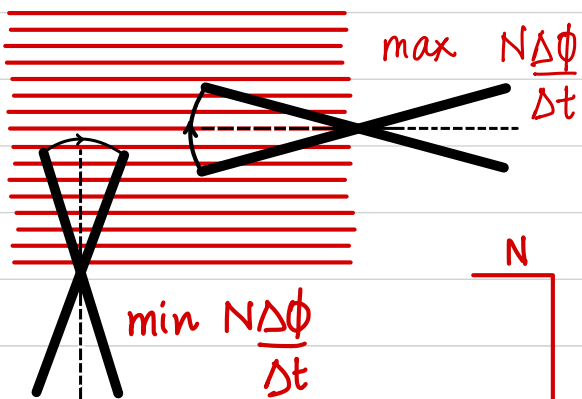
$$\omega = \frac{\theta}{t} \quad \text{and} \quad \theta = \omega t$$




$$V \propto \frac{N \Delta \Phi}{\Delta t}$$

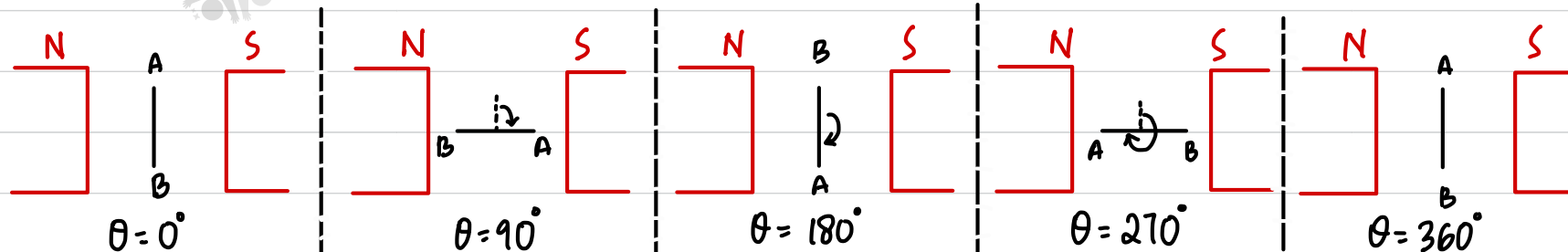
$$V = V_0 \sin \omega t \quad \text{similarly} \quad I = I_0 \sin \omega t$$



Root-Mean-Square Voltage and Current

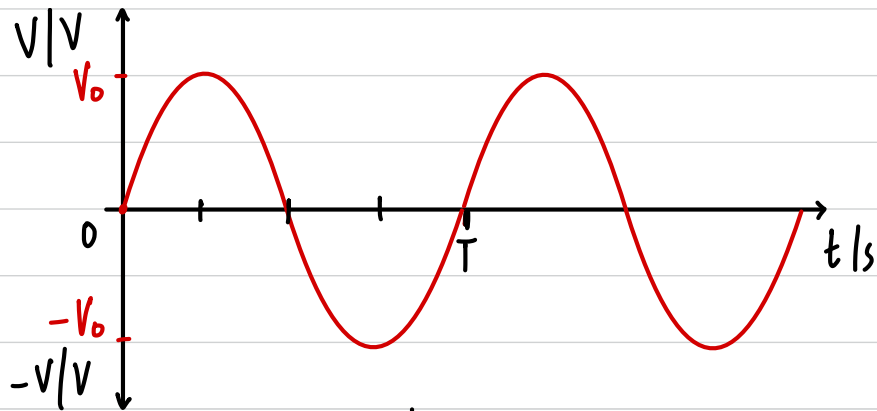

squaring
↓

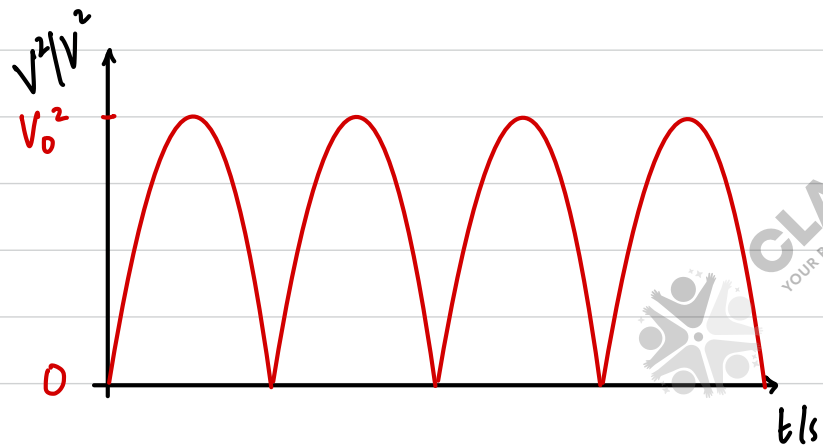

Simple Mean

$$V_{\text{mean}} = \frac{V_0 + (-V_0)}{2} = 0$$

Mean-Square Voltage

$$V_{\text{ms}} = \frac{0 + V_0^2}{2}$$

$$V_{\text{ms}} = \frac{V_0^2}{2}$$

taking square-root,

$$V_{\text{rms}} = \sqrt{\frac{V_0^2}{2}} \quad \text{hence} \quad V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

Similarly for current

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

V_{rms} / I_{rms}

The value of direct voltage / current corresponding to an alternating one that gives the same mean power output as an alternating voltage / current would.

220V AC

OR

$\frac{220}{\sqrt{2}} = 156V$ DC

same mean power output

$$P_{mean} = I_{rms} V_{rms}$$


$$P_{mean} = I_{rms}^2 R$$

$$P_{mean} = \frac{V_{rms}^2}{R}$$

$$P_{max} = I_0 V_0$$

$$P_{mean} = I_{rms} \times V_{rms} \\ = \frac{I_0}{\sqrt{2}} \times \frac{V_0}{\sqrt{2}}$$
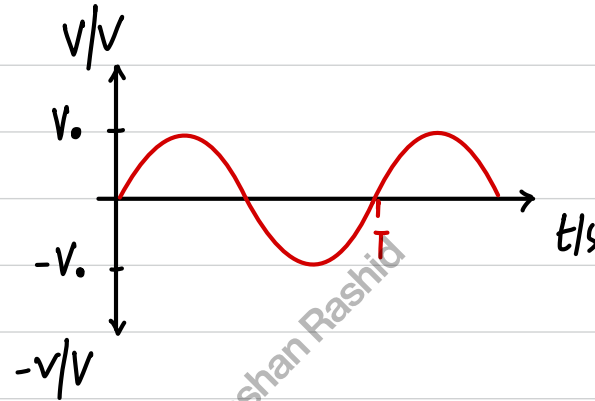
$$P_{mean} = \frac{P_{max}}{2} \quad 50\%$$



$$\text{As } P = IV$$

and

$$V = V_0 \sin \omega t$$



$$I = I_0 \sin \omega t$$


$$P = (V_0 \sin \omega t)(I_0 \sin \omega t)$$

$$P = I_0 V_0 \sin^2 \omega t$$



so

$$P = P_0 \sin^2 \omega t$$

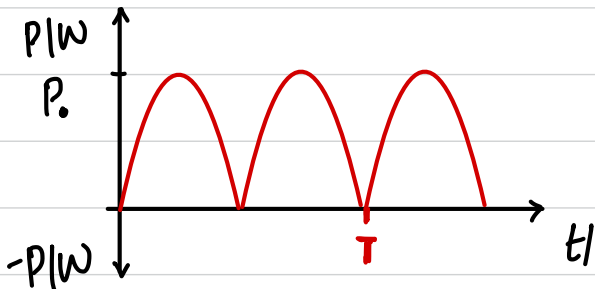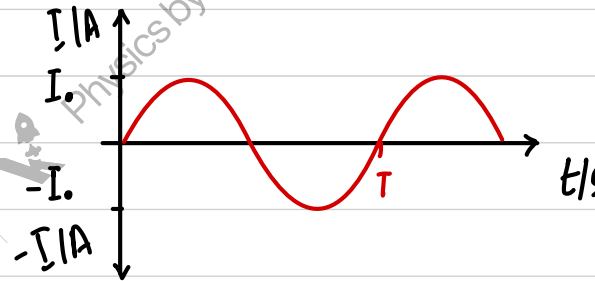

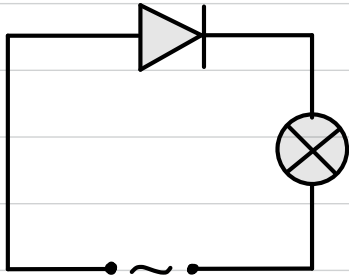


INPUT
SIGNAL

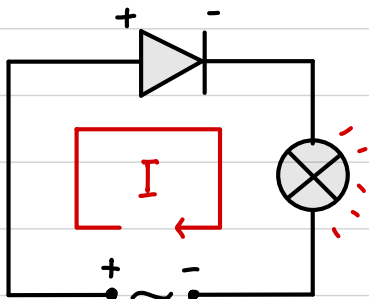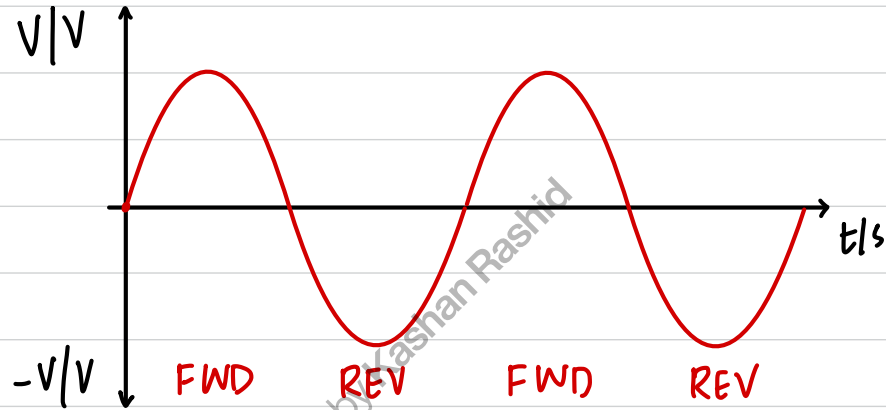

Forward
Biased

All voltage on lamp
No voltage on Diode

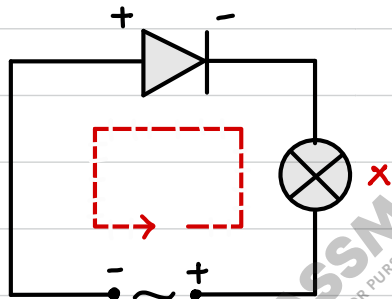

Reversed
Biased

All voltage on Diode
No voltage on Lamp



OUTPUT ON
LAMP


"Rippling DC with Lags"




VOLTAGE
ON DIODE

Full Wave Rectification



Positive Half Cycle


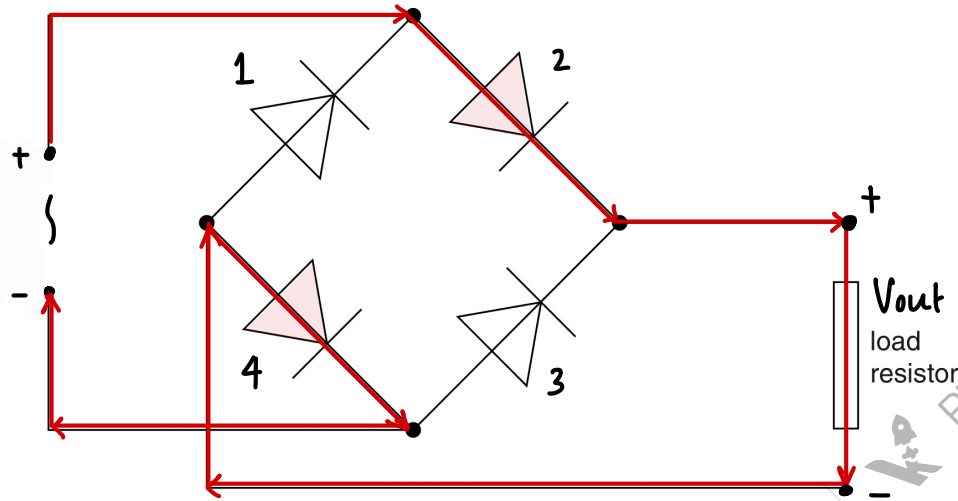


Bridge Rectifier

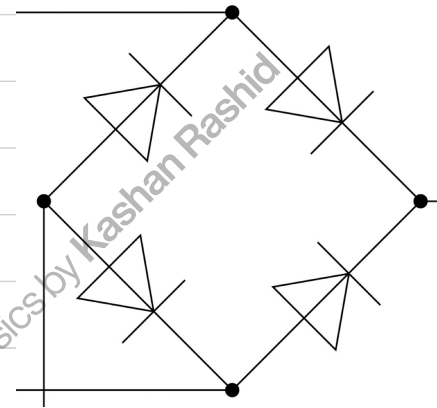



Negative Half Cycle

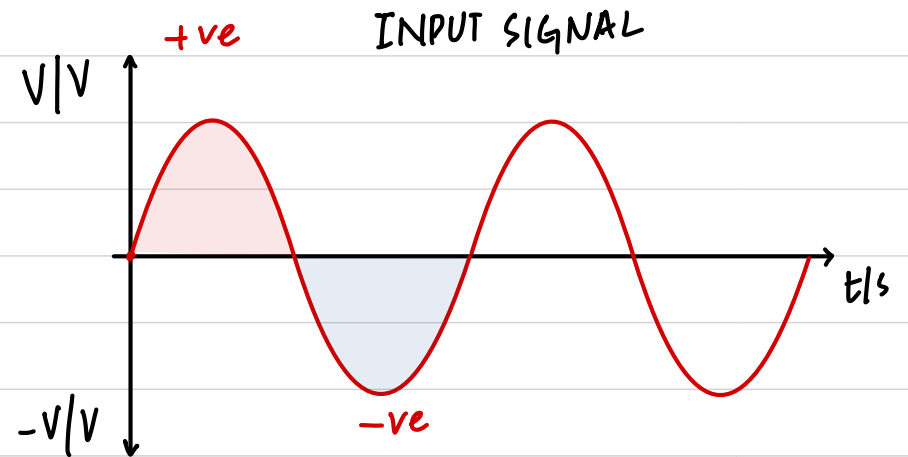
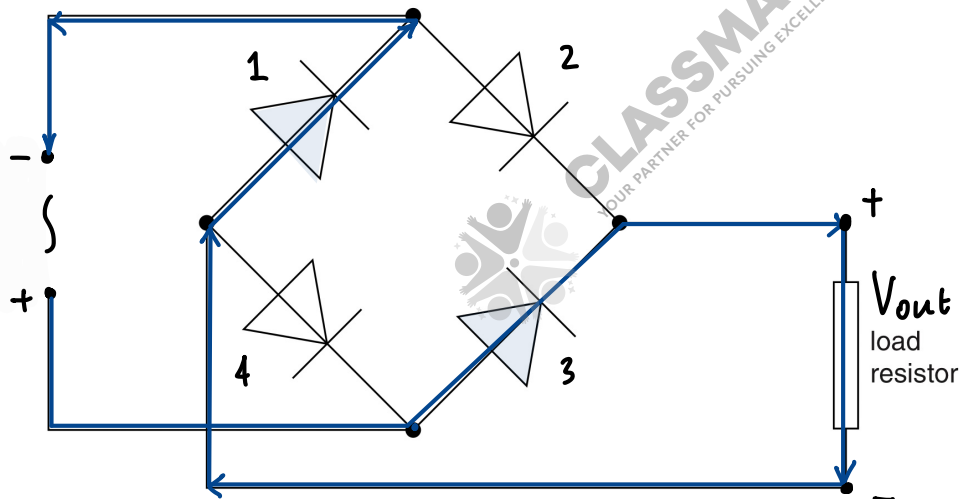


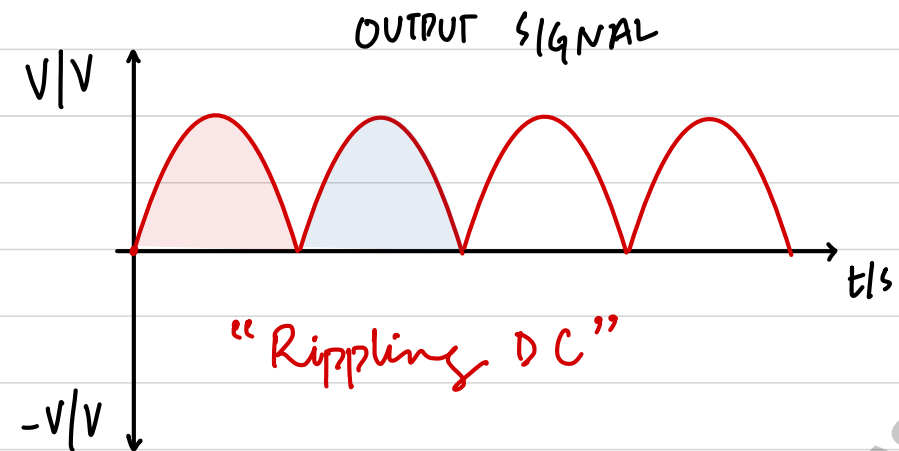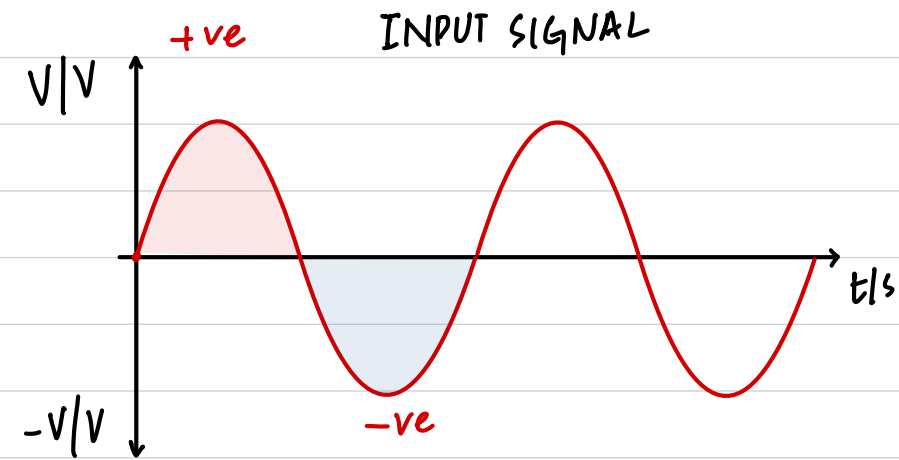

Smoothing

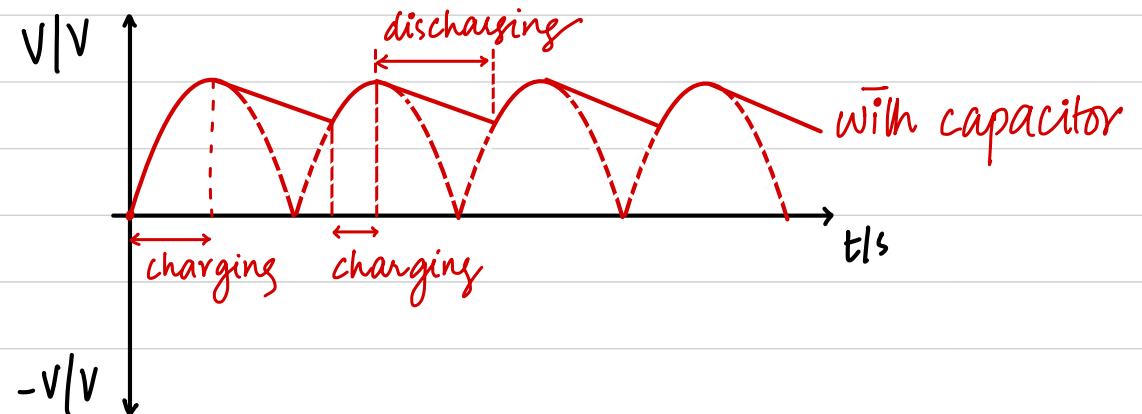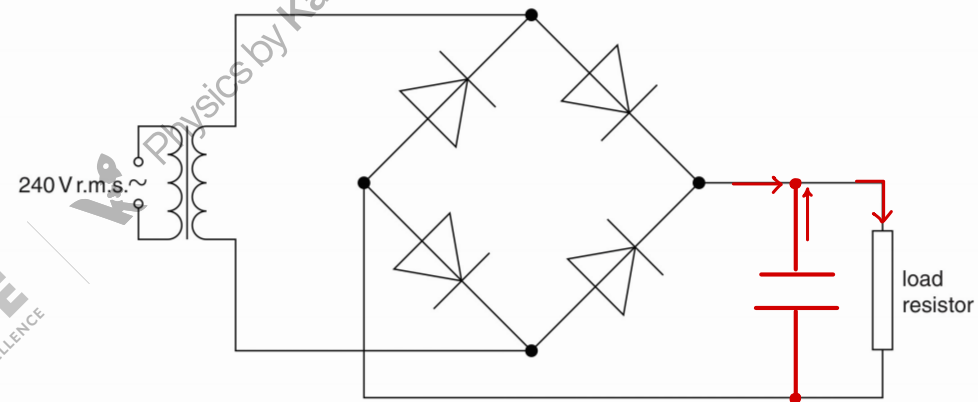Decreasing the drop in the output voltage by attaching a capacitor in parallel to the resistor.



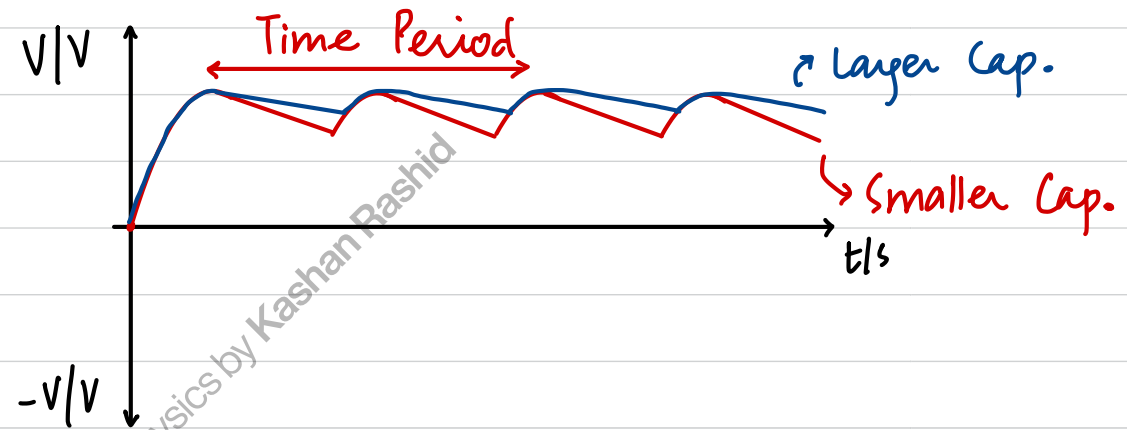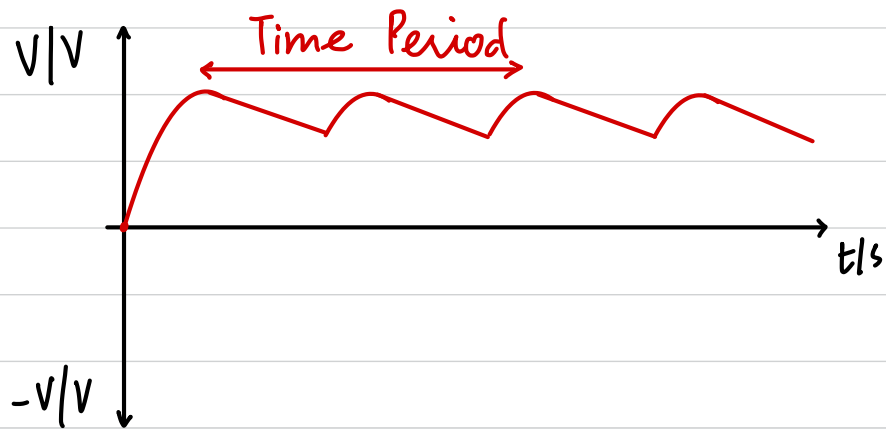

Adding capacitor increases the mean output voltage and hence also increases the mean power output.

"Time Period: 1st crest to 3rd crest in a rectified signal"

- 11 A bridge rectifier contains four ideal diodes A, B, C and D, as shown in Fig. 11.1.

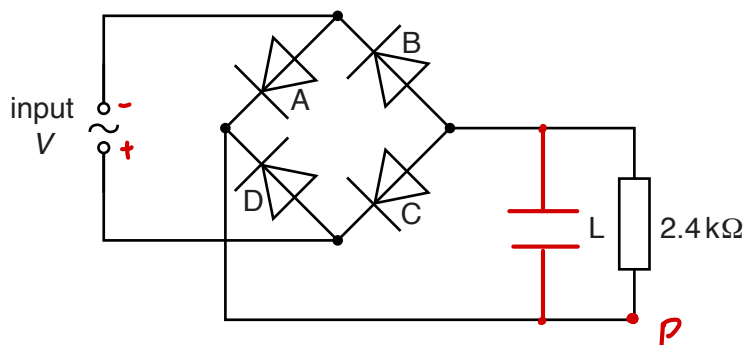


Fig. 11.1

The output of the rectifier is connected to a load L of resistance $2.4\text{ k}\Omega$.

- (a) On Fig. 11.1, mark with the letter P the positive terminal of the load. [1]
- (b) The variation with time t of the potential difference V across the input to the rectifier is shown in Fig. 11.2.

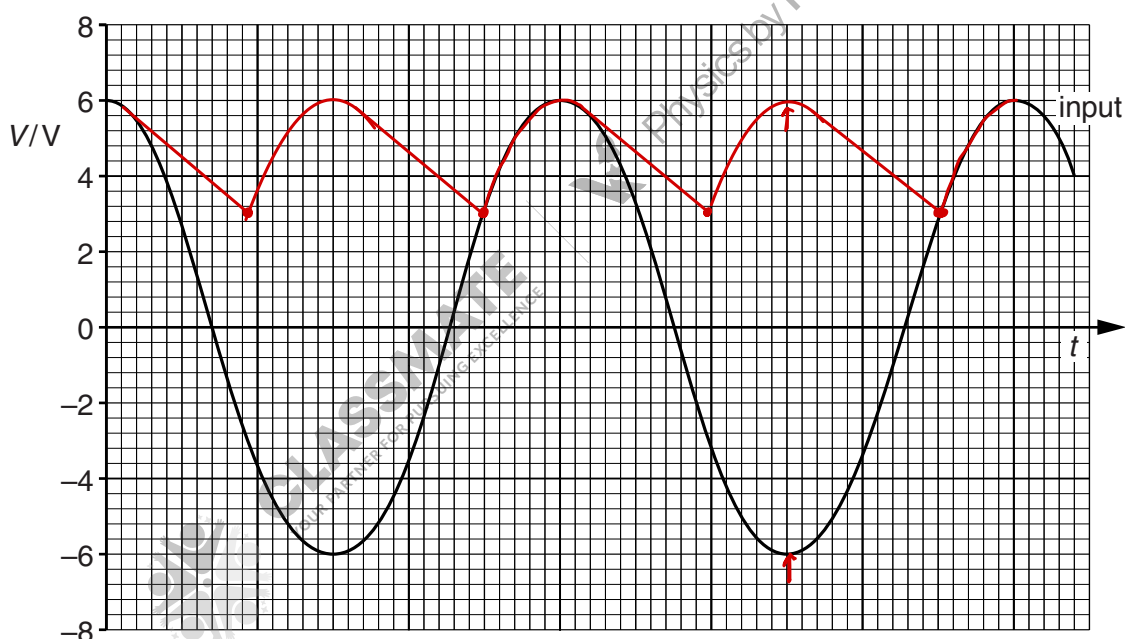


Fig. 11.2

Calculate the root-mean-square (r.m.s.) current in the load L.

$$V_o = I_o R$$

$$6 = I_o (2400)$$

$$I_o = 0.0025\text{ A}$$

$$I_{\text{rms}} = \frac{I_o}{\sqrt{2}}$$

$$= \frac{0.0025}{\sqrt{2}}$$

$$= 0.00177$$

r.m.s. current = 1.78×10^{-3} A [2]

(c) The potential difference across the load L is to be smoothed using a capacitor.

- (i) On Fig. 11.1, draw the symbol for a capacitor, connected to produce smoothing. [1]
- (ii) The minimum potential difference across the load L with the smoothing capacitor connected is 3.0V.

On Fig. 11.2, sketch the variation with time t of the potential difference across the load L .

[3]

[Total: 7]



CLASSMATE
YOUR PARTNER FOR PURSUING EXCELLENCE



Physics by Kashan Rashid